

[4]

SECTION 'C' $4 \times 10 = 40$

Long Answer questions (Word limit 400-450 words.)

UNIT-I

Q. 1. Explain briefly the construction, characteristics and principle of operation of LDR.

OR

What is LED? Give its construction, principle of working and applications.

UNIT-II

Q. 2. Describe the construction and working of a solar cell.

OR

Explain the construction, working and characteristics of photo transistor.

UNIT-III

Q. 3. Draw schematic block diagram of the basic OP-amp with inverting and no-inverting inputs. Sketch their equivalent circuits.

OR

Sketch the circuit diagram of non-inverting amplifier with feedback and determine the expression for closed loop voltage gain, input resistance of OP-amp, with feedback and output resistance with feedback.

UNIT-IV

Q. 4. Describe the functions of an OP-amp as a summing, Scaling and averaging amplifiers.

OR

Describe OP-amp circuits for monostable multivibrator. Explain their operation.

-----xxx-----

[1]

ROLL NO.....

PHY. 204/21

II SEMESTER EXAMINATION, 2021

M.Sc. (PHYSICS)

PAPER-IV

ELECTRONICS-II

TIME: 3 HOURS

MAX.- 80

MIN.- 16

Note: The question paper consists of three sections A, B & C. All questions are compulsory.

Section A- Attempt all multiple choice questions.

Section B- Attempt one question from each unit.

Section C- Attempt one question from each unit.

SECTION 'A' $2 \times 8 = 16$

MCQ (Multiple Choice Questions)

1. Photo conductive device uses :

- (a) metallic conductors
- (b) good quality insulators
- (c) semiconductors
- (d) None of these

2. An LED is :

- (a) an ohmic devices
- (b) a display device
- (c) a voltage regulated device
- (d) All the above

3. In a photo transistor, the photo current is :

- (a) emitter base junction
- (b) collector base junction
- (c) collector
- (d) either (a) or (b)

[2]

4. A photocell solar cell is actually a device which utilises :
- (a) photoconductive effect (b) photovoltaic effect
(c) photoemissive effect (d) photoresistive effect
5. A differential amplifier :
- (a) is a part of an OP-AMP (b) has one input and one output
(c) has two output (d) (a) and (b)
6. The differential gain is :
- (a) very high (b) very low
(c) dependent on input voltage (d) above 100
7. The input offset current equals the -----:
- (a) difference between two base currents
(b) average of two base currents
(c) collector current divided by current gain
(d) None of these
8. The common mode voltage gain is :
- (a) smaller than differential voltage gain
(b) equal to differential voltage gain
(c) greater than differential voltage gain
(d) None of these

[3]

SECTION 'B'

$4 \times 6 = 24$

Short Answer Type Questions (Word limit 200-250 words.)

UNIT-I

- Q. 1.** Explain radiative and non-radiative transition.

OR

Write the advantages and disadvantages of LEDs.

UNIT-II

- Q. 2.** Derive the expression for gain of the photoconductive detector.

OR

Write the advantages and limitations of Solar cells.

UNIT-III

- Q. 3.** Draw the basic circuit of a differential amplifier.

OR

What are common mode and differential mode signals.

UNIT-IV

- Q. 4.** Discuss the two applications of summing amplifiers.

OR

Discuss the operation of an OP-amp integrator.